

EE16A - Lecture 17 Notes

Name: Felix Su SID: 25794773

Spring 2016 GSI: Ena Hariyoshi

Check Negative Feedback

Inverting Amplifier

1. Set any input to 0 (Replace all voltage sources with short circuits, all current sources with open circuits)
2. Dink the output
 - Check how V_{err} and V_{in} are changing (increase/decrease)
 - Positive feedback loop: dink causes V_{out} to slam into a rail
 - Negative Feedback Loop: dink minimized V_{err} and causes V_{out} to track V_{in}
3. Allows you to apply GR 2: $V^+ = V^-$

Check Negative Feedback

Design Example 1 Using only R's & op-amps & voltage sources, implement a current source whose value is proportional to a central voltage

1. State the Goal: Voltage Controlled Current Source (VCCS)
 - Control Voltage (V_c) to create a fixed current ($g_m V_c$ ($g_m = \text{Amps/V}$))
 - Value of current source depends on control voltage
 - 4 terminals (2 terminal for voltage, 2 terminals to create current at the output)
 - 2 separate circuits, but no current between the two circuits
2. Describe a Strategy: Block Diagram
 - Need relationship between voltage and current (Ohm's Law)
 - Measure voltage \rightarrow pass through resistor \rightarrow measure output current
3. Implement the strategy: Voltage Source and Resistor
 - Simplest circuit that satisfies the criteria of the strategy and goal: Voltage source and resistor
 - Only 2 nodes (1 voltage source) - need 4
 - Create additional loop after resistor (at 0 volts to get $I = \frac{V}{R}$ and not allow current to flow into it: OpAmp)
 - OpAmp
 - Connect the circuit after the R to one of the inputs of the OpAmp to divert the current away from ground, but maintain 0I and 0V (O^+)
 - Connect the other input to ground
 - Connect the OpAmp output terminal as the remaining (O^-)
4. Verify That the Strategy Works
 - If you dink the output O^- , the input from the original circuit will always increase, which means it must be V^- and the other has to be V^+ to maintain negative feedback.

- GR1: $I^+ = I^- = 0$; GR 2: $V_c = V_R$ (KVL)
- $I = \frac{V_R}{R} = \frac{V_c}{R}$, By design, I flows through output terminals in original goal ($I = \frac{V_c}{R} = g_m V_c$)
- V_c is not open circuit, like goal wants, so add a buffer (opamp) between voltage source and rest of the circuit